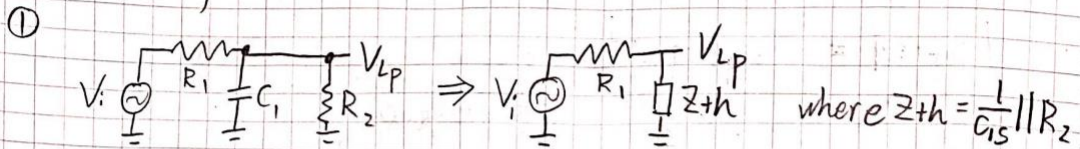


Calculation:

First two pages are calculation for lowpass filter

$$s = j\omega = j2\pi f$$

Lowpass filter:



$$\text{Then } \frac{V_{LP}}{V_i} = \frac{Z_{th}}{R_1 + Z_{th}} = \frac{\frac{1}{sC_1} \parallel R_2}{R_1 + \frac{1}{sC_1} \parallel R_2} = \frac{\frac{\frac{R_2}{sC_1}}{\frac{1}{sC_1} + R_2}}{\frac{1}{sC_1} + R_1 + \frac{R_2}{sC_1} + R_2} = \frac{R_2}{1 + sC_1 R_2} \cdot \frac{R_2}{R_1 + R_2 + \frac{R_2}{sC_1}}$$

$$= \frac{R_2}{R_2 + R_1(1 + sC_1 R_2)} = \frac{R_2}{R_2 + R_1 + sC_1 R_1 R_2} = \frac{R_2}{R_1 + R_2} \left(\frac{1}{1 + \frac{sC_1 R_1 R_2}{R_1 + R_2}} \right)$$

$$\therefore H_{LP}(s) = \frac{V_{LP}}{V_i} = K_L \left(\frac{1}{1 + \frac{s}{\omega_L}} \right)$$

$$\therefore K_L = \frac{R_2}{R_1 + R_2} \quad \& \quad \frac{1}{\omega_L} = \frac{C_1 R_1 R_2}{R_1 + R_2} \Rightarrow \omega_L = \frac{R_1 + R_2}{C_1 R_1 R_2}$$

② Given $f_L = 5 \text{ kHz}$ & $K_L = 0.5$

$$K_L = 0.5 = \frac{R_2}{R_1 + R_2} \Rightarrow 0.5(R_1 + R_2) = R_2 \Rightarrow R_1 + R_2 = 2R_2 \Rightarrow R_1 = R_2$$

$$\therefore f_L = 5 \text{ kHz} \quad \& \quad \omega = 2\pi f$$

$$\therefore \omega_L = \frac{R_1 + R_2}{C_1 R_1 R_2} = 5000 \times 2\pi \Rightarrow \frac{2R_1}{C_1 R_1^2} = 10000\pi \Rightarrow \frac{1}{C_1 R_1} = 5000\pi$$

$$\Rightarrow C_1 R_1 = \frac{1}{5000\pi} = 6.366 \times 10^{-5}$$

Based above equation, assume $R_1 = 1000 \Omega$ & $C_1 = 63.66 \text{ nF}$

Therefore, $R_1 = R_2 = 1 \text{ k}\Omega$ & $C_1 = 63.66 \text{ nF}$


③

$$H_{LP}(s) = K_L \left(\frac{1}{1 + \frac{s}{\omega_L}} \right) = \frac{0.5}{1 + \frac{j\omega}{2\pi \times 5000}} = \frac{5000\pi}{10000\pi + j\omega}$$


$$|H_{LP}(s)| = \frac{5000\pi}{\sqrt{(10000\pi)^2 + \omega^2}} = \frac{5\pi \times 10^3}{\sqrt{\pi^2 \times 10^8 + \omega^2}}$$

$$\angle H_{LP}(s) = -\tan^{-1} \left(\frac{\omega}{10000\pi} \right)$$

magnitude VS ω

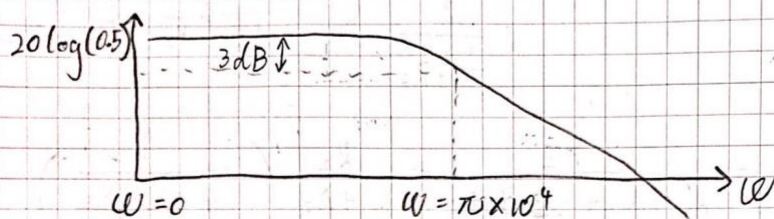

phase vs ω

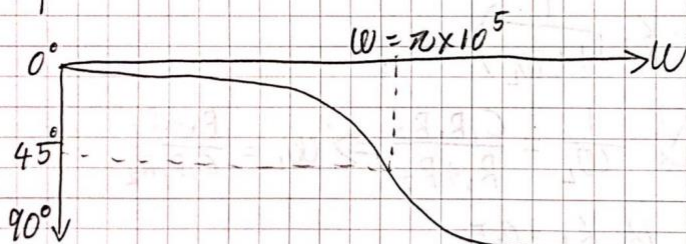

④ Given $V_i(t) = 0.4 \sin(2\pi 4000t)$

$$\omega = 2\pi \times 4000 = 8000\pi$$

$$|H_{LP}(s)| = \frac{5\pi \times 10^3}{\sqrt{\pi^2 \times 10^8 + (8\pi)^2 \times 10^6}} = \frac{5\pi \times 10^3}{\sqrt{164 \times 10^6 \times \pi^2}} = \frac{5}{\sqrt{164}} = 0.390$$

$$\angle H_{LP}(s) = -\tan^{-1} \left(\frac{8000\pi}{10000\pi} \right) = -0.675 \text{ rad}$$

$$V_{LP}(t) = 0.390 \times 0.4 \sin(2\pi 4000t - 0.675) = 0.156 \sin(8000\pi t - 0.675)$$

⑤ $V_i(t) = 0.3 \sin(2\pi 6000t) \Rightarrow \omega = 2\pi \times 6000 = 12000\pi$


$$|H_{LP}(s)| = \frac{5\pi \times 10^3}{\sqrt{\pi^2 \times 10^8 + (12\pi)^2 \times 10^6}} = \frac{5}{\sqrt{244}} = 0.320$$

$$\angle H_{LP}(s) = -\tan^{-1} \left(\frac{12000\pi}{10000\pi} \right) = -0.876$$

$$V_{LP}(t) = 0.32 \times 0.3 \sin(2\pi 6000t - 0.876) = 0.96 \sin(12000\pi t - 0.876)$$

Highpass filter:

highpass filter:

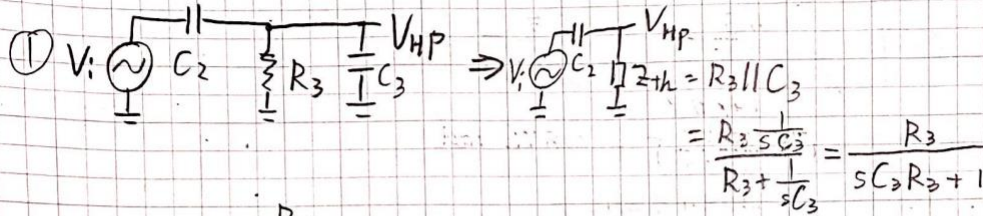

$$\frac{V_{HP}}{V_i} = \frac{\frac{R_3}{sC_3 R_3 + 1}}{\frac{R_3}{sC_3 R_3 + 1} + \frac{1}{sC_2}} = \frac{R_3}{R_3 + \frac{sC_3 R_3 + 1}{sC_2}} = \frac{R_3}{R_3 + \frac{C_3 R_3}{C_2} + \frac{1}{sC_2}}$$

$$\therefore H_{HP}(s) = \frac{V_{HP}}{V_i}(s) = K_H \frac{1}{1 + \frac{\omega_H}{s}} = \left(\frac{R_3}{R_3 + \frac{C_3 R_3}{C_2}} \right) \left(\frac{1}{1 + \frac{1}{sC_2(R_3 + \frac{C_3 R_3}{C_2})}} \right)$$

$$\therefore K_H = \frac{R_3}{R_3 + \frac{C_3 R_3}{C_2}} \quad \& \quad \omega_H = \frac{1}{C_2(R_3 + \frac{C_3 R_3}{C_2})}$$

② $K_H = 0.5$ & $f_H = 5 \text{ KHz} \Rightarrow \omega_H = 10000\pi$

$$K_H = \frac{R_3}{R_3 + \frac{C_3 R_3}{C_2}} = 0.5 \Rightarrow 2R_3 = R_3 + \frac{C_3 R_3}{C_2} \Rightarrow \frac{C_3 R_3}{C_2} = R_3 \Rightarrow C_3 = C_2$$

$$\omega_H = \frac{1}{C_2(R_3 + \frac{C_3 R_3}{C_2})} = \frac{1}{C_2(R_3 + R_3)} = 10000\pi \Rightarrow \frac{1}{C_2 R_3} = 20000\pi$$

$$\Rightarrow C_2 R_3 = \frac{1}{20000\pi} = 15.915 \times 10^{-6}$$

Let $R_3 = 1 \text{ k}\Omega$ & $C_2 = 15.915 \text{ nF}$


So $R_3 = 1 \text{ k}\Omega$ & $C_2 = C_3 = 15.915 \text{ nF}$

③ $H_{HP}(s) = K_H \frac{1}{1 + \frac{\omega_H}{s}} = 0.5 \times \frac{1}{1 + \frac{10000\pi}{j\omega}}$

magnitude: $\frac{0.5}{\sqrt{1 + \frac{10^6 \times \pi^2}{\omega^2}}}$

phase: $\tan^{-1}(\frac{10000\pi}{\omega})$

magnitude vs ω

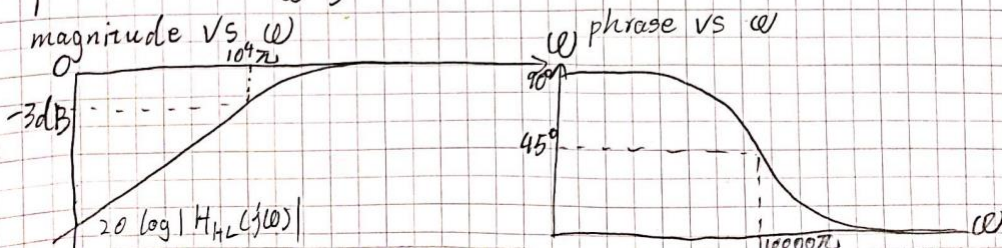

$$\textcircled{4} \quad V_i(t) = 0.4 \sin(2\pi 4000t)$$

$$\omega = 8000\pi$$

$$|H_{HL}(t)| = \frac{0.5}{\sqrt{1^2 + \frac{10^8 \pi^2}{64 \times 10^6 \pi^2}}} = \frac{0.5}{\sqrt{2.5625}} = 0.312$$

$$\angle H_{HL}(t) = \tan^{-1}\left(\frac{10000\pi}{8000\pi}\right) = 0.896 \text{ rad}$$

$$V_{Hp} = 0.3584 \sin(8000\pi t + 0.312)$$

$$\textcircled{5} \quad V_i(t) = 0.3 \sin(2\pi 6000t)$$

$$\omega = 12000\pi$$

$$|H_{HL}(t)| = \frac{0.5}{\sqrt{1^2 + \frac{10^8 \pi^2}{144 \times 10^6 \pi^2}}} = 0.384$$

$$\angle H_{HL}(t) = \tan^{-1}\left(\frac{10000\pi}{12000\pi}\right) = 0.6947 \text{ rad}$$

$$V_{Hp} = 0.1152 \sin(12000\pi t + 0.6947)$$

Schematic:

included both in calculation and simulation


Simulation:

Lowpass filter:

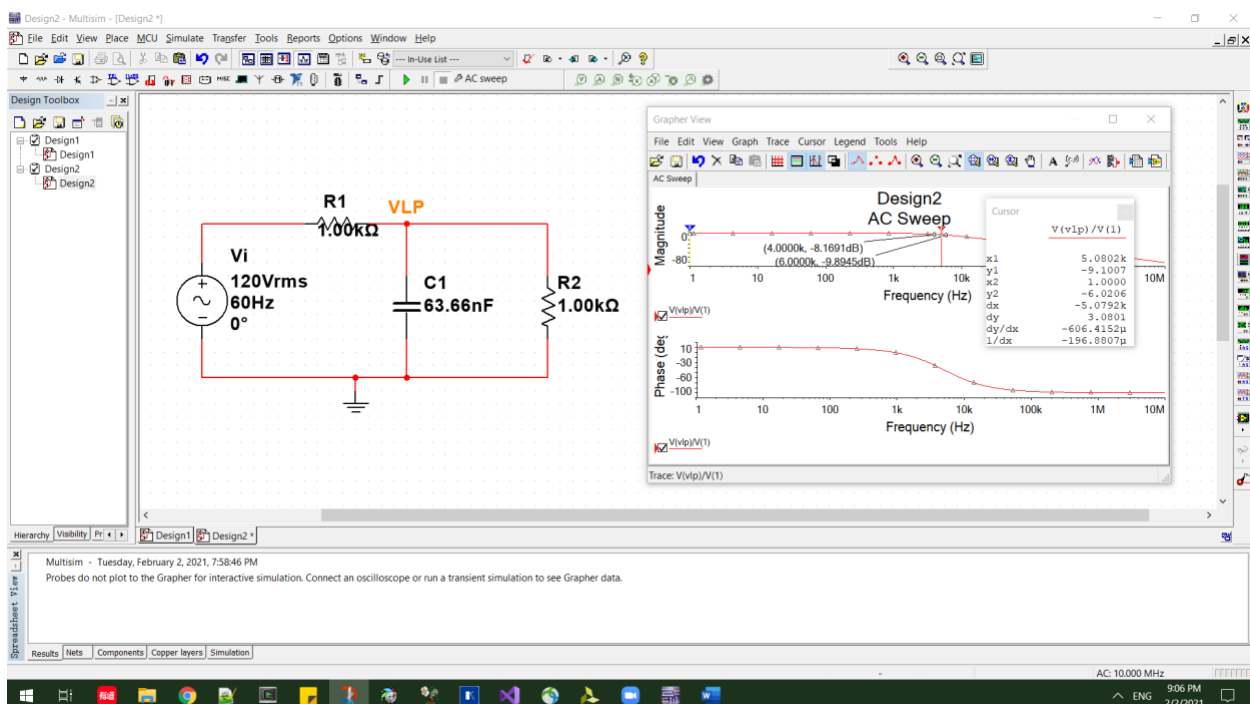1.

3 dB frequency: when dy is around 3, frequency is 5.0802k, and the passband gain is -9.1007 dB

Magnitude at 4kHz and 6kHz: -8.1691dB and -9.8945dB




2. magnitude of input and output are 399.9426mV and 162.2096mV

Phase difference: change in time is 2.3750ms – 2.2769ms = 0.0981ms

$$T = 1 / 4000 = 0.00025s$$
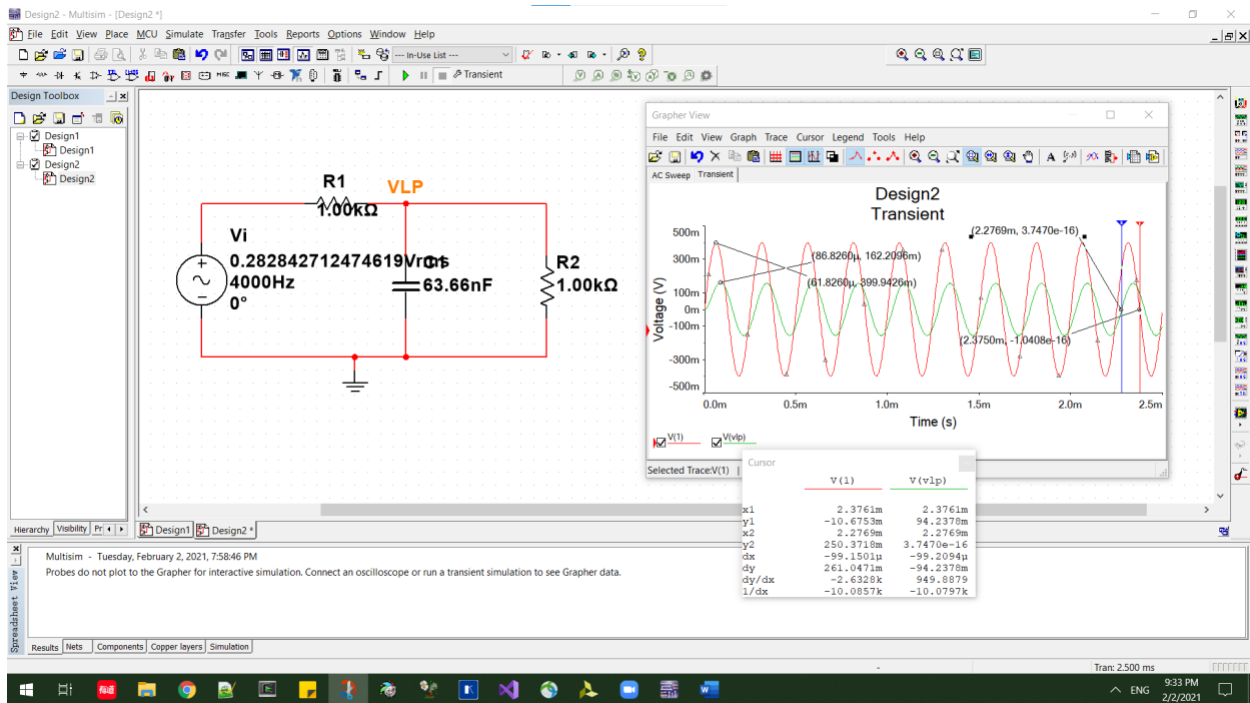
$$\text{Phase difference} = 0.0000981s / 0.00025s * 2\pi = 2.4655\text{rad}$$




3. magnitude of input and output are 299.8579mV and 96.1093mV

Phrase difference: change in time is 1.75ms – 1.8566ms = -.1066ms

$$T = 1 / 6000 = 0.00016667s$$
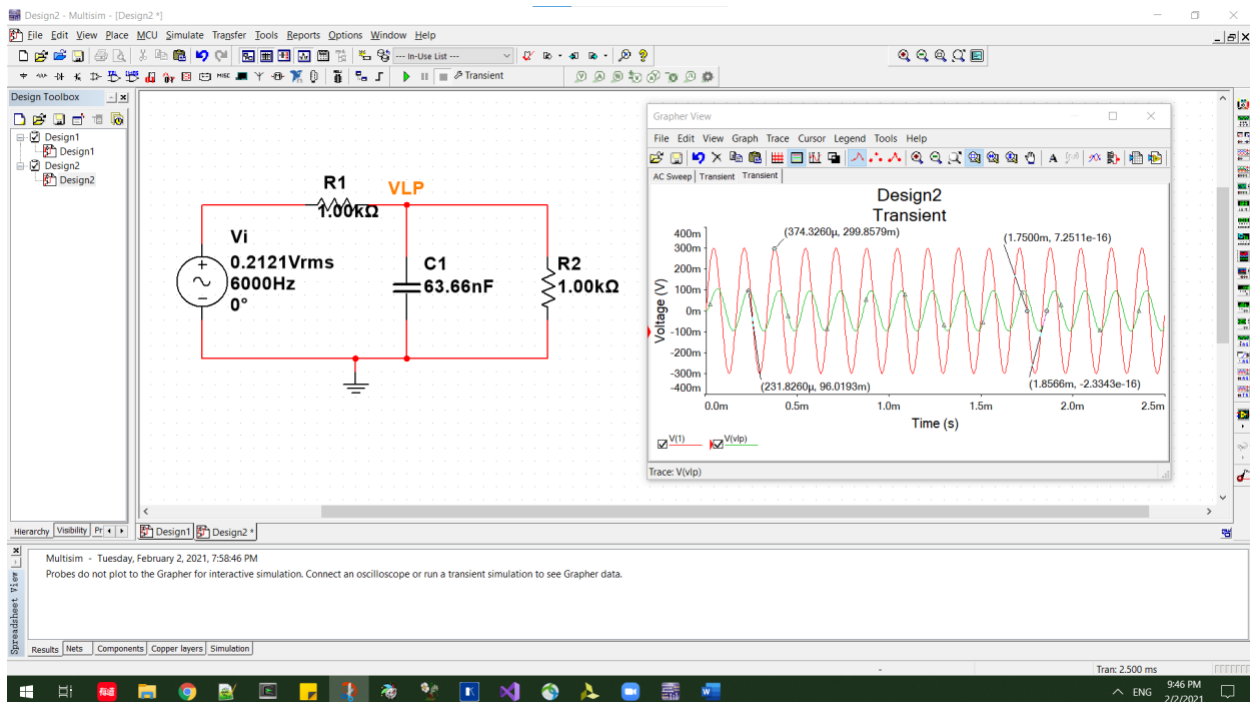
$$\text{Phrase difference} = -0.0001066s / 0.00016667s * 2\pi = -4.0187\text{rad}$$




Highpass filter:

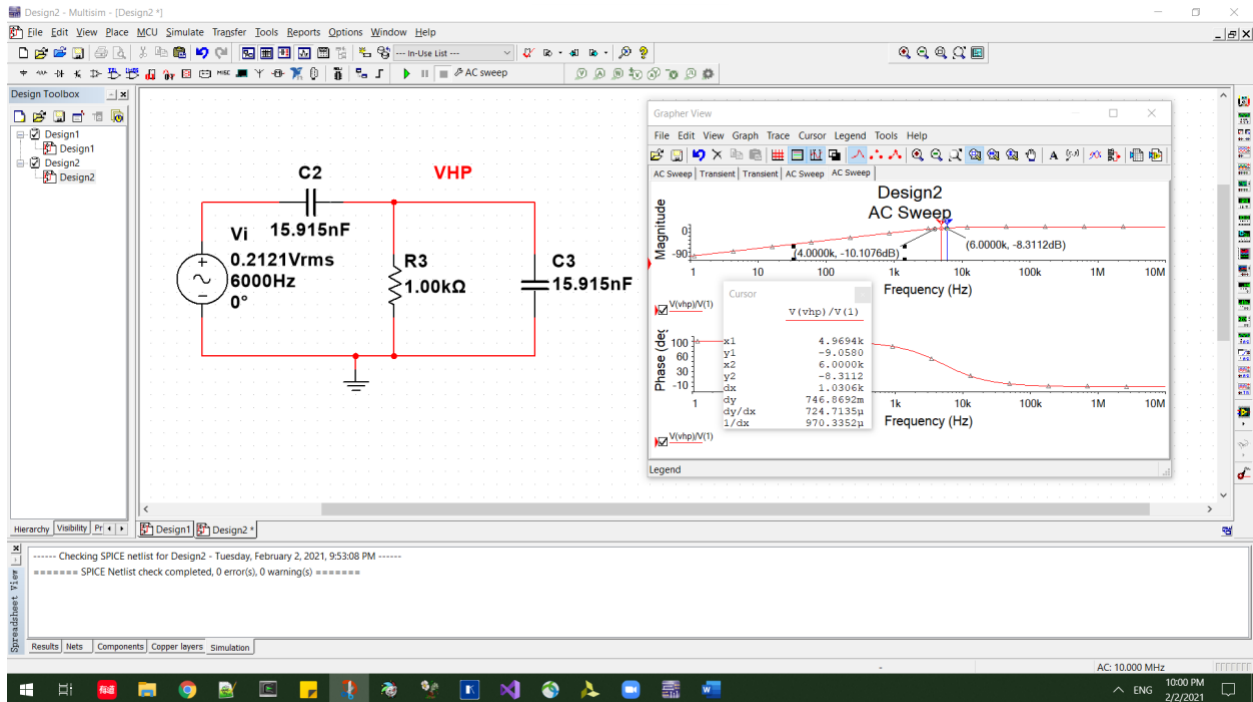1.

3 dB frequency: when dB is around 3, frequency is 4.9694k, and the passband gain is -9.0580 dB

Magnitude at 4kHz and 6kHz: -10.1076dB and -8.3112dB




2. magnitude of input and output are 399.8777mV and 124.8736mV

Phase difference: change in time is $2.1250\text{ms} - 2.0894\text{ms} = 0.0356\text{ms}$

$T = 1 / 4000 = 0.00025\text{s}$

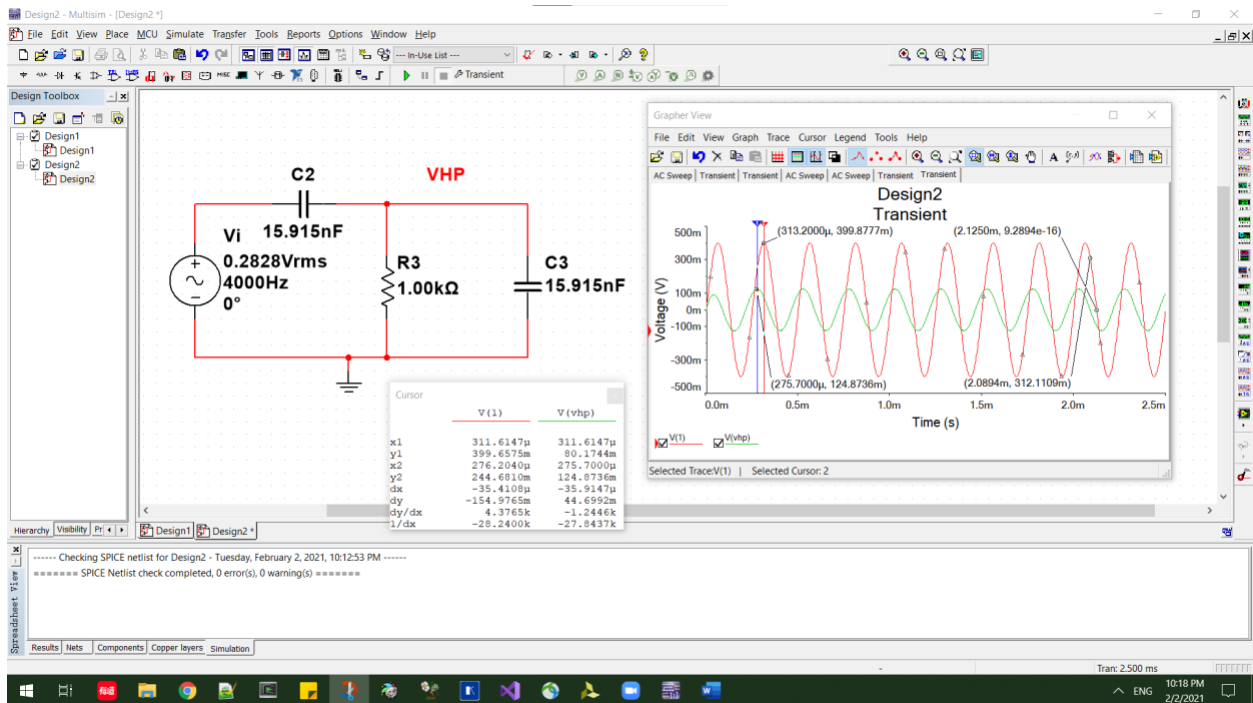Phase difference = $0.000356\text{s} / 0.00025\text{s} * 2\pi = 0.8947\text{rad}$




3. magnitude of input and output are 299.9498mV and 115.1906mV

Phase difference: change in time is 1.3333ms – 1.3149ms = 0.0184ms

$T = 1 / 6000 = 0.00016667s$

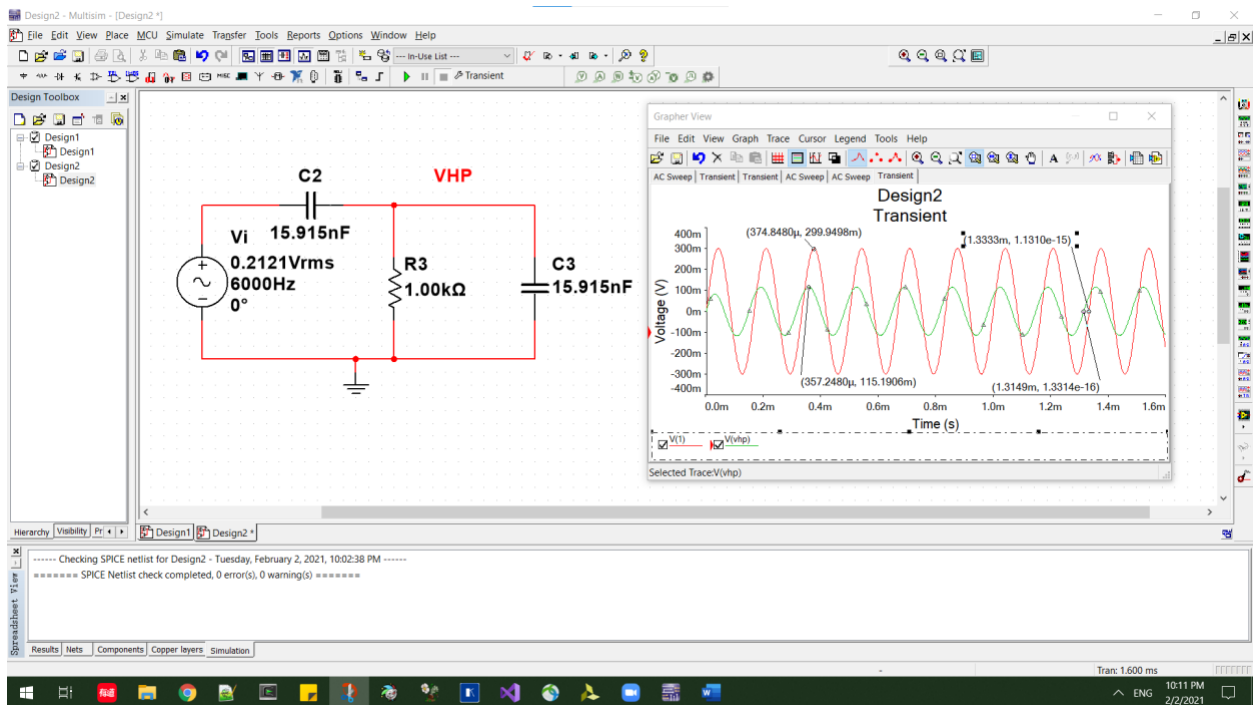Phase difference = $-0.0000184s / 0.00016667s * 2\pi = -0.6936rad$



Measurements:

*since I am not doing in person lab, measurements will be same as simulations

Table, analysis, and conclusion:

For $V_i(t)=0.4\sin(2\pi 4000t)$:

Output voltages	calculated	simulated
lowpass	$0.156\sin(2\pi 4000t-0.675)$	$0.162(2\pi 4000t+2.4655)$
highpass	$0.3584\sin(2\pi 4000t+0.312)$	$0.1248736\sin(2\pi 4000t+0.8947)$

For $V_i(t)=0.3\sin(2\pi 6000t)$:

Output voltages	calculated	simulated
lowpass	$0.96\sin(2\pi 6000t-0.876)$	$0.961093\sin(2\pi 6000t-4.018)$
highpass	$0.1125\sin(2\pi 6000t+0.6947)$	$0.1151906\sin(2\pi 6000t-0.6936)$

Note that phase might be differed by one or two π , which is 3.1415... or 6.2831...

From the comparison, we can see that the magnitude and phase of highpass of $V_i(t)=0.4\sin(2\pi 4000t)$ exists significant difference between calculated and simulated result, the rest of the result matches well with the calculated result. I believe this difference was caused by the choice of cursor.